

CSE435 Introduction to EDA & Testing - Spring 2022

Homework Assignment #5

Shao-Hsuan Chu - B073040018

- (20%) A circuit has the truth table of Table 1. When there is a fault (faults) on the circuit, the faulty truth table becomes Table 2. Try to derive tests to detect the fault (faults).

CD \ AB	AB			
	00	01	11	10
00	1			
01		1	1	
11				1
10			1	1

Table 1

CD \ AB	AB			
	00	01	11	10
00				
01		1	1	
11				
10	1		1	1

Table 2

Solution: Compare two truth tables, we can tell the circuit has stuck-at-0 fault at output when input (A, B, C, D) equals (0, 0, 0, 0) or (1, 0, 1, 1). The circuit also has stuck-at-1 fault at output when the input equals (0, 0, 1, 0).

Answers: {(0, 0, 0, 0), (1, 0, 1, 1), (0, 0, 1, 0)}

- (80%) Generate a test for the fault f-sa1 in Figure 1 by the following FOUR methods. Be sure to give the **key steps to show the features of every algorithm**, and also **draw the decision trees** for each case.

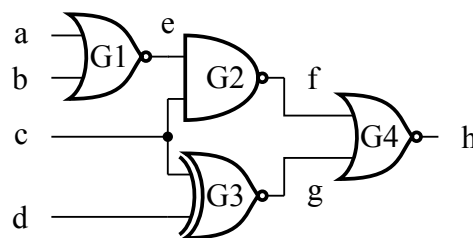


Figure 1

- (20%) Use the **Boolean difference method** to derive all the test patterns to detect the fault f-sa1.

Solution: To test the stuck-at-1 fault at f , f must equal 0 to activate the fault. In addition, the fault has to be observable at the output, meaning that the boolean difference of the logic function F w.r.t. f should be 1, i.e., $F_f(0) \oplus F_f(1) = 1$.

$$\begin{aligned}
f &= 0 \\
f' &= 1 \\
F_f(0) \oplus F_f(1) &= 1 \\
(f')(F_f(0) \oplus F_f(1)) &= 1 \\
(f')(0 + (c \oplus d)')' \oplus (1 + (c \oplus d)')' &= 1 \\
(f')(c \oplus d \oplus 0) &= 1 \\
(f')(c \oplus d) &= 1 \\
((a + b)'c)''(c \oplus d) &= 1 \\
((a + b)'c)(c \oplus d) &= 1 \\
a'b'c(c \oplus d) &= 1 \\
a'b'c(cd' + c'd) &= 1 \\
a'b'ccd' + a'b'cc'd &= 1 \\
a'b'cd' &= 1
\end{aligned}$$

Answer: $\{(a, b, c, d) \mid a'b'cd' = 1\} = \{(0, 0, 1, 0)\}.$

(b) (20%) Generate a test for the fault f-sa1 by using **D-algorithm**.

Solution:

Step	Decision	Implication	Comment
1	f = D'	e = c = 1 a = b = 0	Activate f-sa1 (ce)' = 0 (a+b)' = 1
2	g = 0	h = D d = 0	Propagate via h c ⊕ d = 1, and c = 1 (from step 1)

Answer: (a, b, c, d) = (0, 0, 1, 0).

(c) (20%) Generate a test for the fault f-sa1 by using **9-V Algorithm**.

Solution: Same as 2(b) above.

(d) (20%) Generate a test for the fault f-sa1 by using **PODEM algorithm**.

Solution:

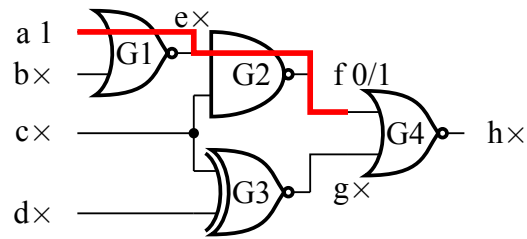


Figure 2: Activate f-sa1, so $f = 0$. Objective = $(f, 0)$, inversion parity = even. Therefore, $a = f = 0$.

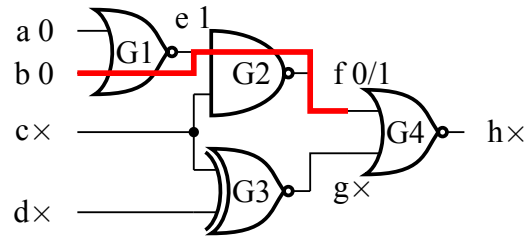


Figure 3: Objective = $(f, 0)$, inversion parity = even. Therefore, $b = f = 0$, $e = 1$.

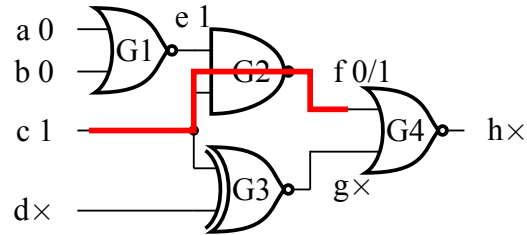


Figure 4: Objective = $(f, 0)$, inversion parity = odd. Therefore, $c = f' = 1$

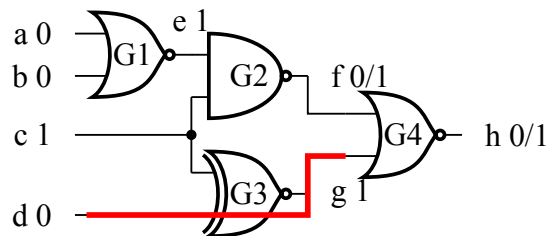


Figure 5: To propagate to h, $g = 1$. Objective = $(g, 1)$, inversion parity = odd. Therefore, $d = g' = 0$. f-sa1 is now observable at h, thus complete.

Answer: $(a, b, c, d) = (0, 0, 1, 0)$.