

CSE435 Introduction to EDA & Testing - Spring 2022

Homework Assignment #5

Shao-Hsuan Chu - B073040018

1. (20%) A circuit has the truth table of Table 1. When there is a fault (faults) on the circuit, the faulty truth table becomes Table 2. Try to derive tests to detect the fault (faults).

		AB			
		00	01	11	10
CD	00	1			
	01		1	1	
	11				1
	10			1	1

Table 1

		AB			
		00	01	11	10
CD	00				
	01		1	1	
	11				
	10	1		1	1

Table 2

Solution: Compare two truth tables, we can tell the circuit has stuck-at-0 fault at output when input (A, B, C, D) equals (0, 0, 0, 0) or (1, 0, 1, 1). The circuit also has stuck-at-1 fault at output when the input equals (0, 0, 1, 0).

Answers: {(0, 0, 0, 0), (1, 0, 1, 1), (0, 0, 1, 0)}

2. (80%) Generate a test for the fault f-sa1 in Figure 1 by the following FOUR methods. Be sure to give the **key steps to show the features of every algorithm**, and also **draw the decision trees** for each case.

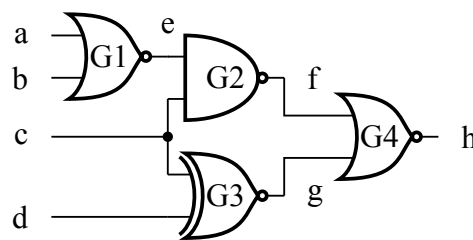


Figure 1

- (a) (20%) Use the **Boolean difference method** to derive all the test patterns to detect the fault f-sa1.

Solution: To test the stuck-at-1 fault at f , f must equal 0 to activate the fault. In addition, the fault has to be observable at the output, meaning that the boolean difference of the logic function F w.r.t. f should be 1, i.e., $F_f(0) \oplus F_f(1) = 1$.

$$\begin{aligned}
f &= 0 \\
f' &= 1 \\
F_f(0) \oplus F_f(1) &= 1 \\
(f')(F_f(0) \oplus F_f(1)) &= 1 \\
(f')(0 + (c \oplus d)') \oplus (1 + (c \oplus d)') &= 1 \\
(f')(c \oplus d \oplus 0) &= 1 \\
(f')(c \oplus d) &= 1 \\
((a + b)'c)''(c \oplus d) &= 1 \\
((a + b)'c)(c \oplus d) &= 1 \\
a'b'c(c \oplus d) &= 1 \\
a'b'c(cd' + c'd) &= 1 \\
a'b'ccd' + a'b'cc'd &= 1 \\
a'b'cd' &= 1
\end{aligned}$$

Answer: $\{(a, b, c, d) \mid a'b'cd' = 1\} = \{(0, 0, 1, 0)\}.$

(b) (20%) Generate a test for the fault f-sa1 by using **D-algorithm**.

Solution:

Step	Comments	Cube							
		a	b	c	d	e	f	g	h
1	Activate f-sa1. $TC(0) = PDCF$			1		1	D'		
2	Backward implication: SC_{G1} $TC(1) = TC(0) \cap SC_{G1}$	0	0			1			
		0	0	1		1	D'		
3	Propagate fault. D-drive = G4. PDC_{G4} $TC(2) = TC(1) \cap PDC_{G4}$						D'	0	D
		0	0	1		1	D'	0	D
4	Backward implication: SC_{G3} $TC(3) = TC(2) \cap SC_{G3}$			1	0			0	
		0	0	1	0	1	D'	0	D
5	No justification needed. Test generated.								

Answer: $(a, b, c, d) = (0, 0, 1, 0).$

(c) (20%) Generate a test for the fault f-sa1 by using **9-V Algorithm**.

Solution: Same as 2(b) above.

(d) (20%) Generate a test for the fault f-sa1 by using **PODEM algorithm**.

Solution:

1. Activate f-sa1. Initial objective: $f = 0$.
2. Since G2 is an imply gate, backtrace to the hardest PI, a. With an even inversion parity, $a = 0$. Simulation, objective not achieved.
3. Backtrace to the next hardest PI, b. With an even inversion parity, $b = 0$, $e = 1$. Simulation, objective not achieved.
4. Backtrace to the next hardest PI, c. With an old inversion parity, $c = 1$. Simulation, objective achieved.
5. Propagate the fault. Objective: $g = 0$.
6. Backtrace to the remaining PI, d. With an old inversion parity, $d = 1$. Simulation, $g = (c \oplus d)' = 0$. Conflict with the objective. Flip d to 0. Simulation, objective achieved.
7. Test generated, $(a, b, c, d) = (0, 0, 1, 0)$.

Answer: $(a, b, c, d) = (0, 0, 1, 0)$.